

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER- 1st / 2nd EXAMINATION (New Syllabus) – WINTER 2013

Subject Code: 2110005

Date: 24-12-2013

Subject Name: Element of Electrical Engineering

Time: 10:30 am – 01:00 pm

Total Marks: 70

Instructions:

1. Question No. 1 is compulsory. Attempt any four out of remaining six questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1 Objective Question

(a) **07**

1. Define : rms value for alternating circuit.
2. Three equal resistance of magnitude 5 Ohm each are connected in delta. The resistance between any two pair of terminals of the delta will be _____ ohms.
3. Write Lenz law.
4. Define power factor.
5. The Q factor of coil is given by _____.
6. A 12Ω resistor, a $40 \mu\text{F}$ capacitor, and an 8 mH coil are in series across an ac source. The resonant frequency is _____.
7. To tune a parallel resonant circuit to a higher frequency, the capacitance should be

(b) **07**

1. Write any one similarity between electric and magnetic circuit.
2. The R.M.S. value of a half wave rectified sinusoidal alternating current with peak value I_m is _____.
3. Write function of 'fuse' in electrical circuit.
4. The 'gauss' is unit of _____.
5. Write ohm's law.
6. The five $0.050\mu\text{F}$ capacitors are connected in parallel. The equivalent capacitance is _____.
7. Define luminance

Q.2 (a) Establish relationship between line and phase voltages and currents in balanced delta connection. Draw complete phasor diagram of voltages and currents. **07**

(b) Explain series resonance circuit. Draw resonance curve. **07**

Q.3 (a) An inductive coil of resistance R and inductance L is connected in parallel with capacitor of C. Derive an expression for the resonant frequency and Q factor. **07**

(b) An iron ring has mean diameter of 57.3 cm. It carries a coil having 450 turns and the current flowing through coil is 2 A. The relative permeability of the iron is 1200. Calculate the flux density produced. **07**

Q.4 (a) Define temperature co-efficient of resistance. How does the resistance of different materials vary with temperature? **07**

Prove that $\alpha_t = \alpha_0 / (1 + \alpha_0 t)$ and $\alpha_2 = 1 / [(1 / \alpha_1) + (t_2 - t_1)]$

- (b) Three capacitors having capacitances of $10\ \mu\text{F}$, $20\ \mu\text{F}$ and $40\ \mu\text{F}$ are connected in series to a $400\ \text{V}$ d.c. source. Find (i) total capacitance (ii) total charge in circuit (iii) total energy stored. **07**
- Q.5** (a) Derive the expression for the decay of current in an inductive circuit. Define time constant. **07**
- (b) A coil resistance $15\ \Omega$ and inductance $0.05\ \text{H}$ is connected in parallel with a non-inductive resistance of $20\ \Omega$. The circuit is connected across $200\ \text{V}$, $50\ \text{Hz}$ supply. Determine (i) current in each branch (ii) total current supplied (ii) power factor of the combination. **07**
- Q.6** (a) Prove that current in purely capacitive circuit leads its voltage by 90° and average power consumption in pure capacitor is zero. **07**
- (b) A delta connected load having branch impedances of $(15 + j20)\ \Omega$ is connected to a $220\ \text{V}$, 3 phase AC supply. Find **07**
- Line currents.
 - Per phase power consumed.
 - What is the phasor sum of the line currents? Why does it have this value?
- Q.7** (a) Explain construction of cable in detail. **07**
- (b) Short note on ELCB **07**
